

# EXPERIMENT 5 REPORT

## BBM233 LOGIC DESIGN LABORATORY

**Name and Surname :** Meltem Kaya  
**Student ID :** 21827555  
**Due Date :** 26/12/2020



HACETTEPE  
University

Department of Computer  
Engineering

—


**Teaching Assistant**  
Selma Dilek

## Table of Contents

1. Problem Statement.....	3
2. State Transition Table.....	4
3. Number of Flip Flops.....	4
4. Input Output Equations.....	4
5. Karnaugh Maps.....	5
6. Design Schematic.....	6
7. Dflipflop.v.....	6
8. controller.v.....	7
9. controller_tb.v.....	7
10. Obtained Waveform.....	8
11. Explanations.....	8
12. <b>Resources</b> .....	<b>8</b>

## SOFTWARE DESIGN NOTES

### Problem Statement

 

The state diagram of a control unit is shown in figure above. It has four states, two inputs x and y, and one 2-bit output F. Use D flip flops as storage elements to store the state information. Implement the design in Verilog using structural design approach. Main purpose of this experiment is designing and simulating a sequential circuit by using D flip flops.

---

## State Transition Table

Present State		Next State		Flip Flop Inputs		Output F	
A	B	$A^+$	$B^+$	x	y	$F_2$	$F_1$
0	0	0	0	0	X	0	0
0	0	0	1	1	X	0	0
0	1	1	0	X	0	0	1
0	1	1	1	X	1	0	1
1	0	0	0	0	X	1	0
1	0	1	0	1	0	1	0
1	0	1	1	1	1	1	0
1	1	0	0	0	X	1	1
1	1	1	0	1	0	1	1
1	1	1	1	1	1	1	1

Note: **X** -> Don't cares

$B^+$  -> Next state B

$A^+$  -> Next state A

## Number of D-Flip Flops Needed to Store the State Information

We need two D-Flip Flops to store state information because the number of states is four.

# Evaluating Output Functions by Using Karnaugh Map

xy	00	01	11	10
AB				
00	0	0	0	0
01	1	1	1	1
11	1	1	1	1
10	0	0	0	0

## Simplifying $F_1$ Function

$$F_1 = B$$

xy	00	01	11	10
AB				
00	0	0	0	0
01	0	0	0	0
11	1	1	1	1
10	1	1	1	1

## Simplifying $F_2$ Function

$$F_2 = A$$

xy	00	01	11	10
AB				
00	0	0	0	0
01	1	1	1	1
11	0	0	1	1
10	0	0	1	1

## Simplifying $A^+$ Function


$$A^+ = A'B + Ax$$

xy	00	01	11	10
AB				
00	0	0	1	1
01	0	1	1	0
11	0	0	1	0
10	0	0	1	0

## Simplifying $B^+$ Function

$$B^+ = A'B'x + A'By + xy$$

## Design Schematic

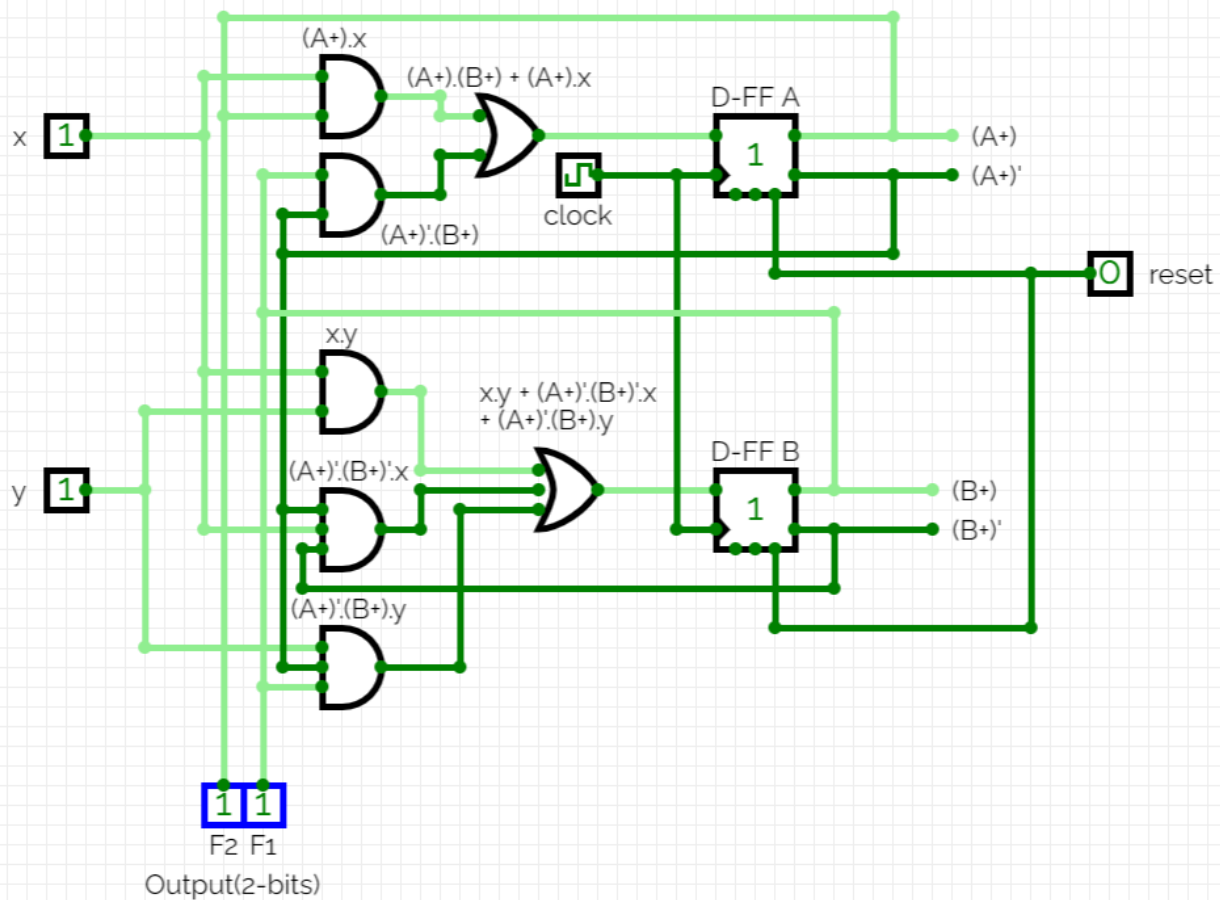

## Dflipflop.v

```

1  `timescale 1ns / 1ps
2
3  module Dflipflop(
4  output reg Q,
5  input D,
6  input clk,rst // clk -> clock, rst -> reset
7  );
8  always @(posedge clk,posedge rst) begin
9
10     if (rst)
11         Q <= 1'b0; //if reset is 1, assign output to 0
12
13     else
14         Q <= D; //non-blocking assign statement, assign output to D
15 end
16 endmodule

```


## controller.v

```
1 `timescale 1ns / 1ps
2 `include "Dflipflop.v"
3
4 module controller(
5     output [1:0]F, // 2-bits output
6     input x, y, clk,reset // clk -> clock
7 );
8
9     reg [1:0] present_state = 2'b0; // initialization of present state with 2'b00 value
10    wire [1:0] next_state; // declaration of next_state
11
12    Dflipflop D2(.Q(next_state[1]),.D(~present_state[1] & present_state[0] | present_state[1] & x),.clk(clk),.rst(reset));
13    Dflipflop D1(.Q(next_state[0]),.D(~present_state[1] & ~present_state[0] & x | ~present_state[1] & present_state[0] & y | x & y),.clk(clk),.rst(reset));
14
15    always @ (next_state) begin
16
17        present_state <= next_state; // updating present state
18    end
19    assign F = present_state; //assign output
20
21
22 endmodule
23
```

## controller\_tb.v

```
1 `timescale 1ns / 1ps
2 `include "controller.v"
3
4 module controller_tb;
5
6     reg x,y,clk,rst; // x,y -> inputs , clk -> clock, rst -> reset
7     wire [1:0]F_tb; // 2-bits output
8
9     controller UUT(.F(F_tb),.x(x),.y(y),.clk(clk),.reset(rst)); //unit under test
10
11     initial begin
12         rst = 1'b1; //initialization reset
13         clk = 1'b0; //initialization clock
14         #50 rst= 1'b0; //set reset to 0
15         #550 $finish;
16     end
17
18     always #25 clk = ~clk; //clock generator. period of clock is 50
19
20     always begin
21         #50 {x,y} = 2'b10; //test inputs.
22         #50 {x,y} = 2'b01;
23         #50 {x,y} = 2'b10;
24         #50 {x,y} = 2'b11;
25         #50 {x,y} = 2'b11;
26         #50 {x,y} = 2'b01;
27         #50 {x,y} = 2'b00;
28         #50 {x,y} = 2'b10;
29         #50 {x,y} = 2'b10;
30         #50 {x,y} = 2'b10;
31         #50 {x,y} = 2'b00;
32     end
33 endmodule
```

## Obtained Waveform

 

## Explanations

We can see that it is a Moore Machine from state diagram, means that output depends on only current state. If we look obtained waveform, we can see that all possible transitions are used to confirm whether circuit design is working correctly.

Reset equals to 1 between 0-50.000ns. In that range, inputs are not initialized. From 50.000 to 600.000ns reset equals to zero and we can see all possible transitions by the same line with positive edges of clock and outputs equal to present state.

## Resources

TOBB ETU University Logic Design Lecture Records

BBM233 Lecture records and documents

<https://www.youtube.com/watch?v=X75NM8eNzro>

<https://mil.ufl.edu/3701/classes/joel/16%20Lecture.pdf>

[https://en.wikipedia.org/wiki/State-transition\\_table](https://en.wikipedia.org/wiki/State-transition_table)

<https://www.sciencedirect.com/topics/computer-science/moore-machine>